

University of Dhaka  
Affiliated Engineering Colleges  
B. Sc. in Computer Science & Engineering  
2<sup>nd</sup> Year 1<sup>st</sup> Semester Final Examination-2021  
CSE 2103 (Digital Electronics & Pulse Technique)

Time: 3.00 Hours

Marks: 70

[Answer any Five questions]

- 
- |  |   |
|--|---|
| 1. a) What is Switch? Draw a two-input NAND and NOR gate circuit using diode.  | 6 |
| b) Define Transistor. "Diode can be used as a switch"- show graphically with characteristic curve.                         | 4 |
| c) Explain RTL basic circuits.   | 4 |
|  |   |
| 2. a) Explain classification of logic family.  | 3 |
| b) Draw the Transistor Transistor Logic (TTL) circuit and explain working procedure.                                       | 5 |
| c) What is pulse transformer? Write the functions of pulse transformer.  | 6 |
|  |   |
| 3. a) What do mean by LED and LCD?   | 4 |
| b) Explain Sample and Hold (S/H) circuit by using Operational Amplifier.   | 5 |
| c) Describe Analog to digital Converter circuit.   | 5 |
|  |   |
| 4. a) Write short Note on- i) Propagation delay ii) Noise margin   | 4 |
| b) Define filtering. Why filtering needed in linear wave shaping?  | 4 |
| c) Explain high pass filter circuit with proper diagrams.  | 4 |
| d) Sketch the frequency response of low pass filter.   | 2 |
|  |   |
| 5. a) Define clipper and clamper circuits. Write down the applications of clipping circuit.                                | 5 |
| b) - Define free running multivibrator. Describe the working principles of positive clipping circuit with proper diagrams. | 5 |
| c) Differentiate between negative diode clipping and negative biased diode clipping circuits with figures.                 | 4 |
|  |   |
| 6. a) Draw the block diagram of a D/A converter and explain its operation.   | 6 |
| b) Mention the process of triggering of a bistable multivibrator with proper diagram.                                      | 4 |
| c) Define PLA's working principles. Write down the applications of S/H circuits.   | 4 |
|  |   |
| 7. a) What is Cache Memory? Differentiate between primary and secondary memory.  | 4 |
| b) Explain pulse generator block diagram with equivalent circuit.  | 5 |
| c) What is OP-AMP. Why OP-AMP is a differential, voltage amplifier with high gain?   | 5 |


University of Dhaka  
Affiliated Engineering Colleges  
B. Sc. in Computer Science & Engineering  
2<sup>nd</sup> Year 1<sup>st</sup> Semester Final Examination-2021  
EEE 2104 (Electronic Devices and Circuits)

Time: 3.00 Hours


Marks: 70

[Answer any Five questions]

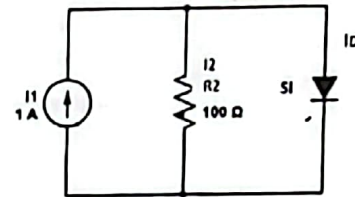
1. a) What is semiconductor? Write down properties of semiconductor. 3  
 b) Why we use semiconductor? Discuss about intrinsic semiconductor. 5  
 c) What is LED? Explain working principle of LED. 4  
 d) What do you mean by extrinsic semiconductor? 2
2. a) What is diode? Explain operating principle of bridge full wave rectifier. 5  
 b) Discuss V-I characteristics of PN junction. 6  
 c) Determine the currents  $I_2$ , and  $I_D$  for the network of Figure. 3



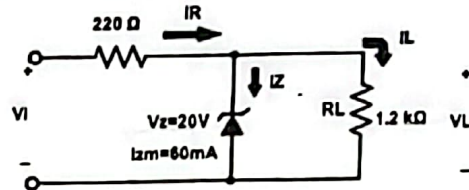3. a) How Zener diode works as voltage regulator. Write down application of diode. 4  
 b) What do you mean by clippers & clampers circuit? 2  
 c) Write down advantage and disadvantage of full wave rectifier. 4  
 d) For the Zener diode network of Figure. Determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ . Where  $V_i = 30$  V. 4



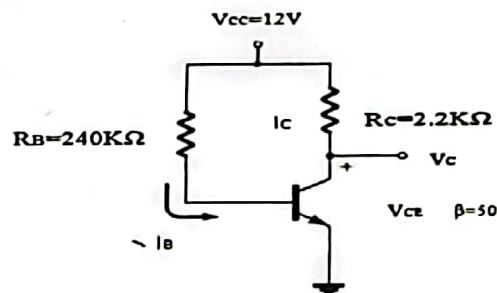4. a) What do you mean by leakage current? 1  
 b) Explain CE characteristics of transistor. 5  
 c) Discuss about Transistor Circuit as an amplifier. 3  
 d) Determine the following for the fixed-bias configuration of Figure. 5  
 (i)  $I_B$  and  $I_C$ .  
 (ii)  $V_{CE}$ .  
 (iii)  $V_B$  and  $V_C$ .  
 (iv)  $V_{BC}$ .



5. a) Write down the advantages of FET over BJT. 2  
 b) Discuss working principle of JFET with necessary diagram. 7  
 c) Explain the circuit operation of E-MOSFET according to Threshold voltage. 5
6. a) What is Operational Amplifier? Write the properties of it. 1+2  
 b) For inverting Amplifier derive the equation given below, 7  

$$A_{cl} = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$
  
 c) Find the output voltage for the circuit shown in Fig. 4


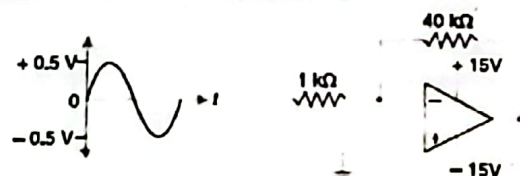


Fig.

7. a) For the input wave to the clipping circuit shown in Fig., find the output waveform.

7

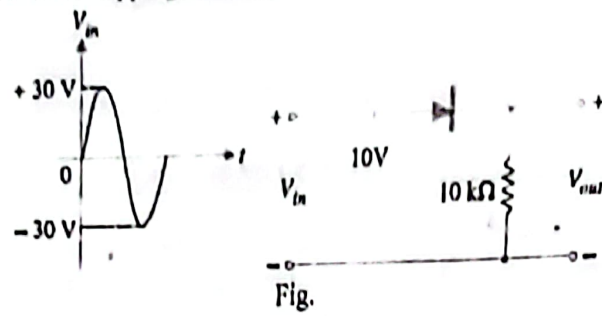

- b) For the input waveform to the clipping circuit in Fig., find the output voltage waveform.

7

